

Recent Advances (from Munich) in Dealing with Process Variations

Ulf Schlichtmann

Contributions: Christoph Knoth, Veit Kleeberger, Bing Li,
Manuel Schmidt

Institute for Electronic Design Automation
Technische Universität München


Outline

- Timing Analysis of Digital Circuits
- Statistical Waveform Variation Propagation
- Current Source Models (Transfer System Models)
- Summary

Outline



- Timing Analysis of Digital Circuits
- Statistical Waveform Variation Propagation
- Current Source Models (Transfer System Models)
- Summary

Static Timing Analysis in a Nutshell

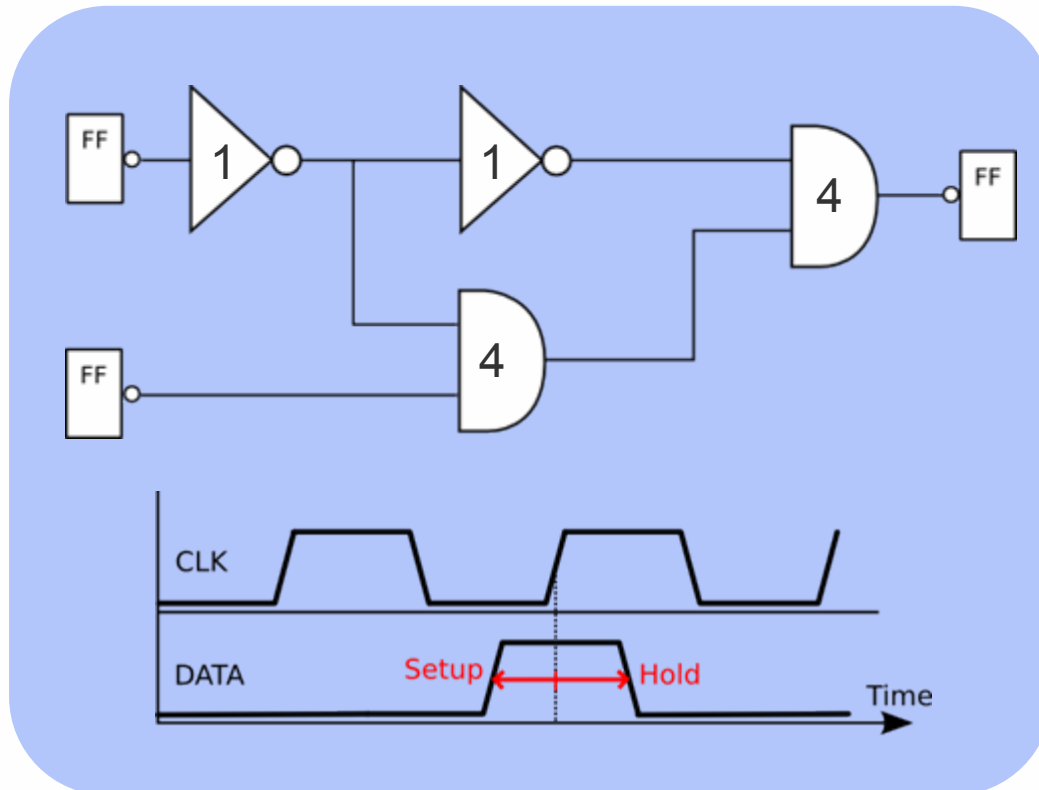

- neglect logic function
- find longest/shortest path
- check for setup and hold time violations

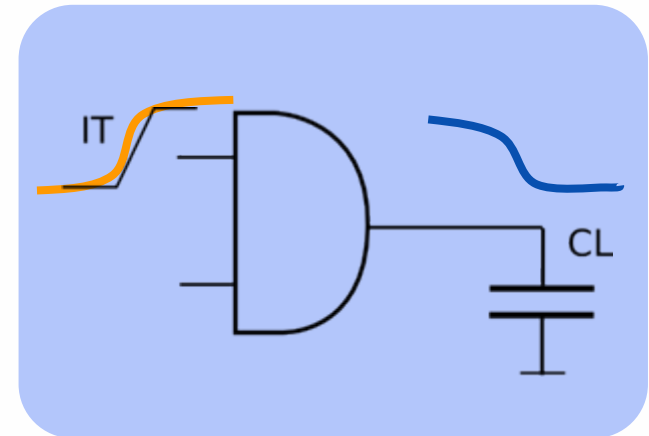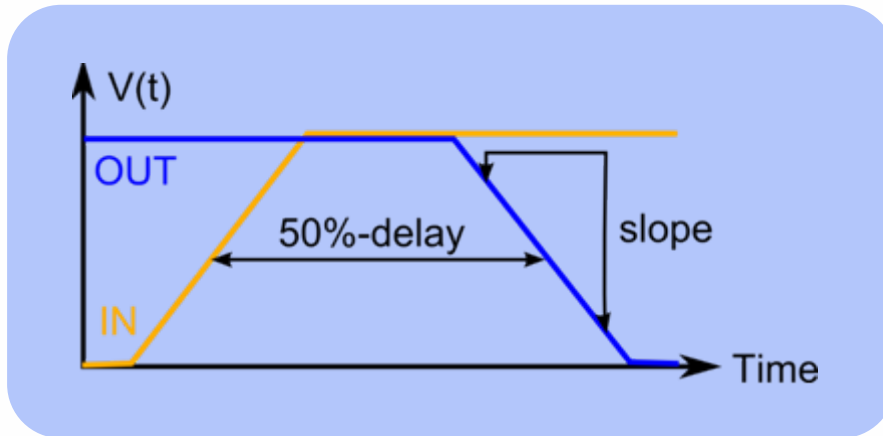Gate delays from pre-characterized Look-up Table




$$\text{Delay/OT} = \begin{bmatrix} & \text{CL} & \rightarrow & & \\ \text{IT} & 1.0 & 2.0 & 4.0 & 6.0 \\ \downarrow & 1.2 & 2.1 & 4.2 & 6.0 \\ & 1.4 & 2.3 & 4.3 & 6.1 \\ & 1.6 & 2.5 & 4.4 & 6.2 \end{bmatrix}$$


- Parameters:
Slope (IT),
Load Capacitance (CL)

Relevance of Waveforms

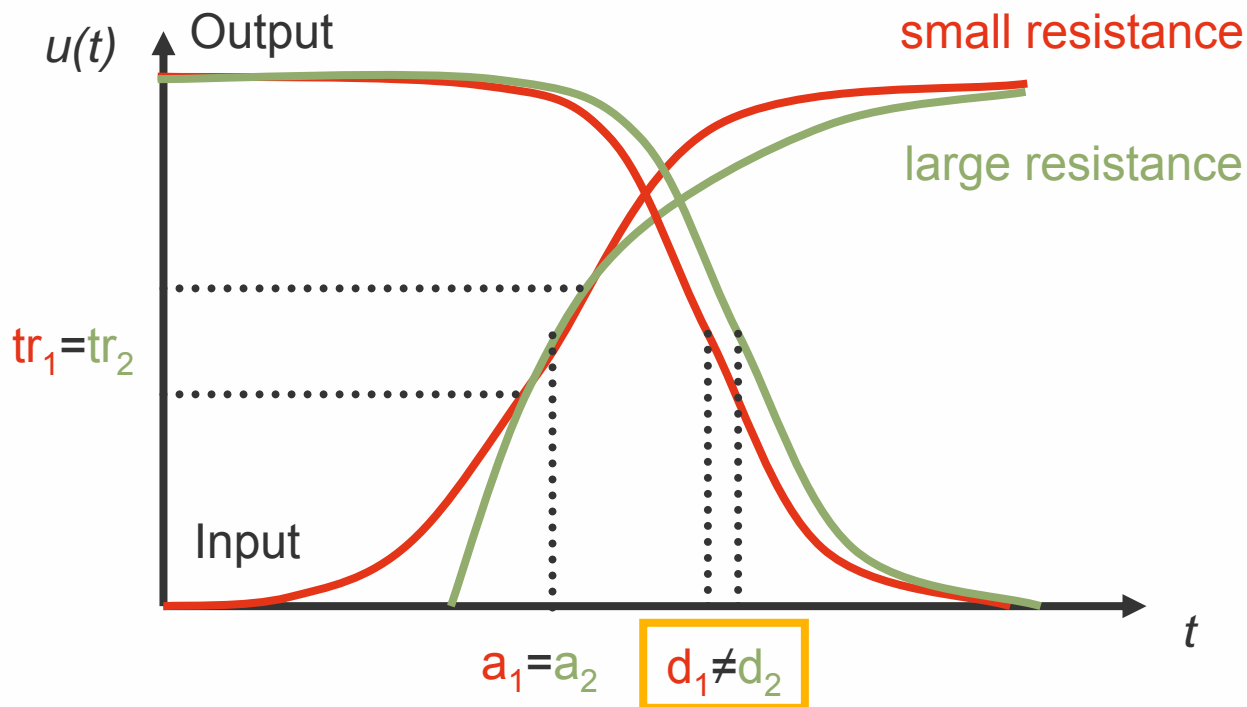- increasing resistive shielding from wiring
- today's standard modeling does not capture resulting effects




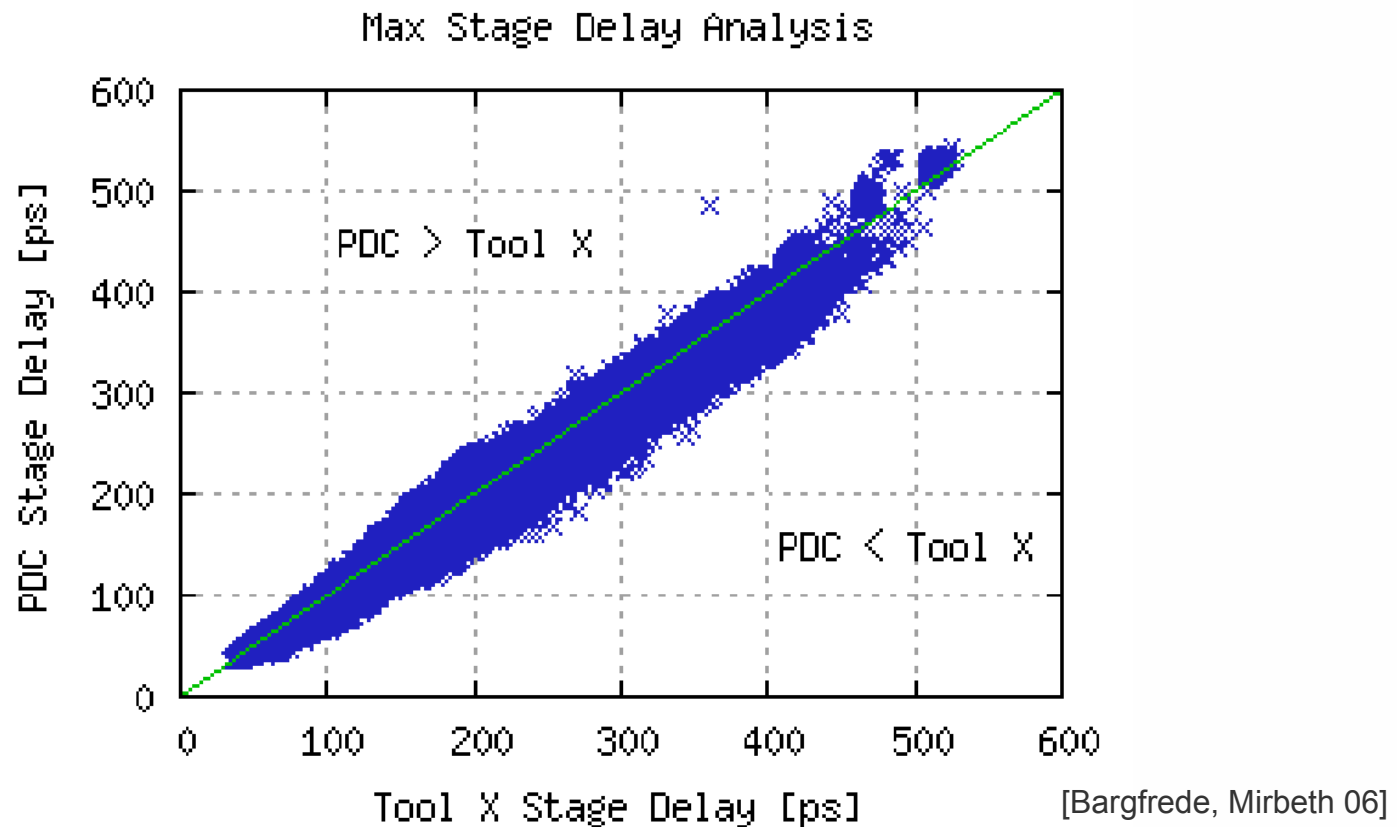Effects of too simplistic modeling: inaccuracy



3-Sigma Variations of Technology Parameters

variations relative to nominal values

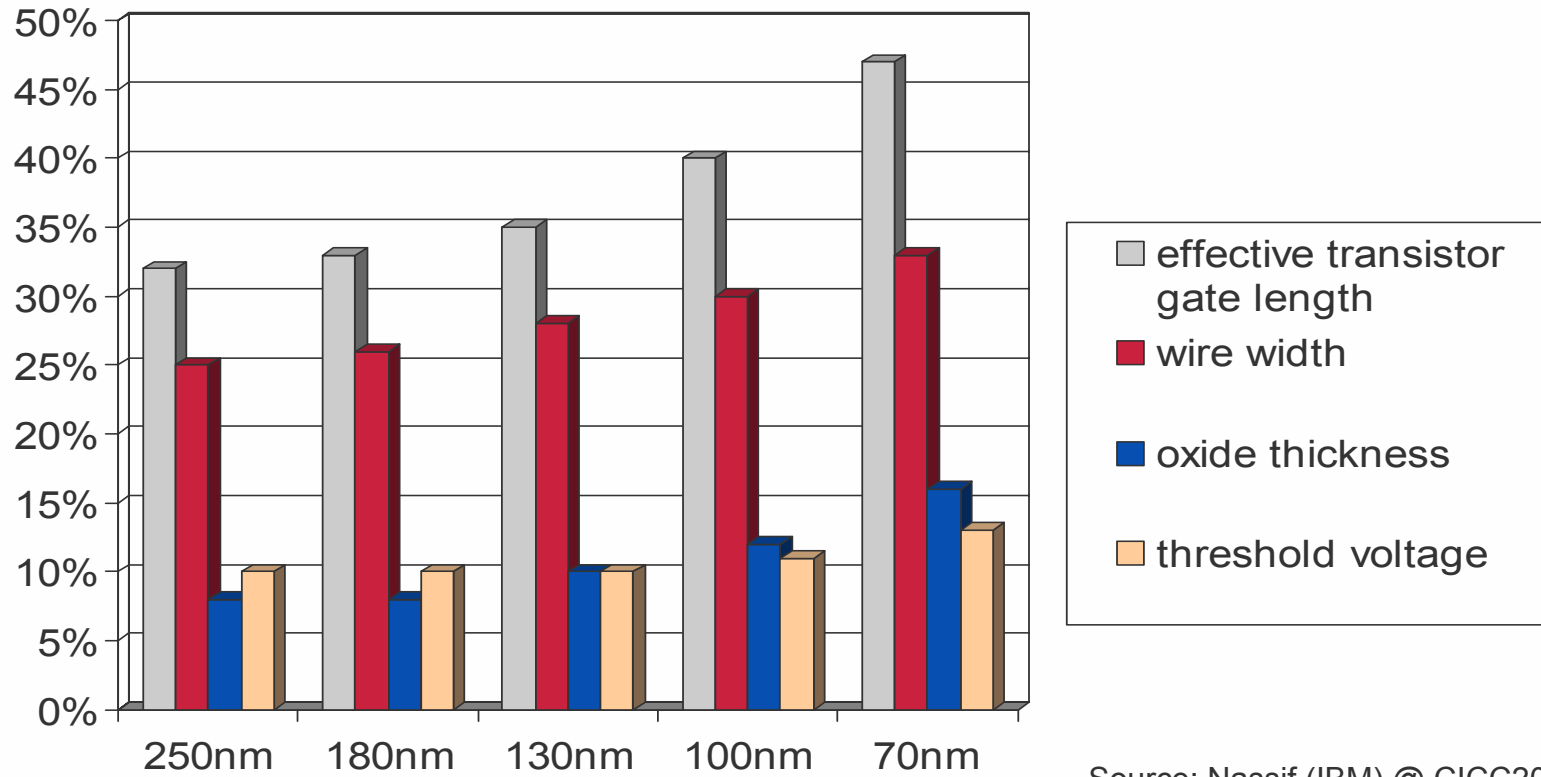


Source: Nassif (IBM) @ CICC2001

Outline

- Timing Analysis of Digital Circuits
- Statistical Waveform Variation Propagation
- Current Source Models (Transfer System Models)
- Summary

Path Delay Calculator (Infineon) [Bargfrede, Mirbeth 06]

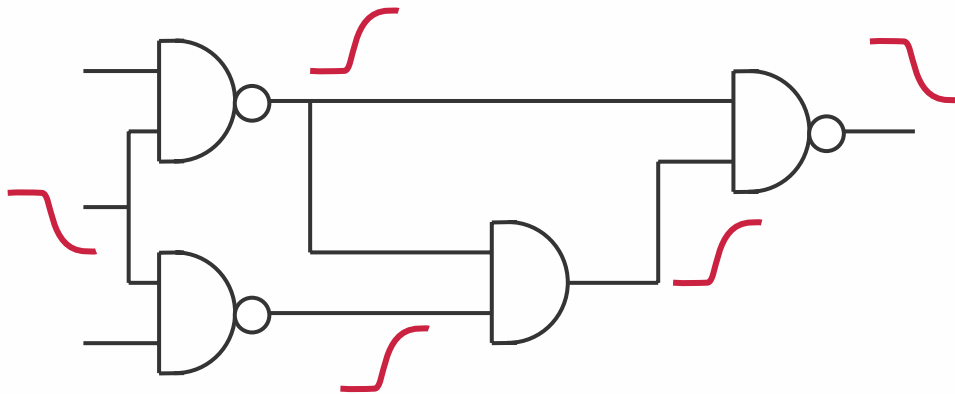
- Block-based timing reference tool
- Successive analog simulations
- Entire dynamic load taken into account
- Propagation of analog waveforms



Static timing analysis

- SPICE-like accuracy
- much faster

Trade-off between Runtime and Accuracy

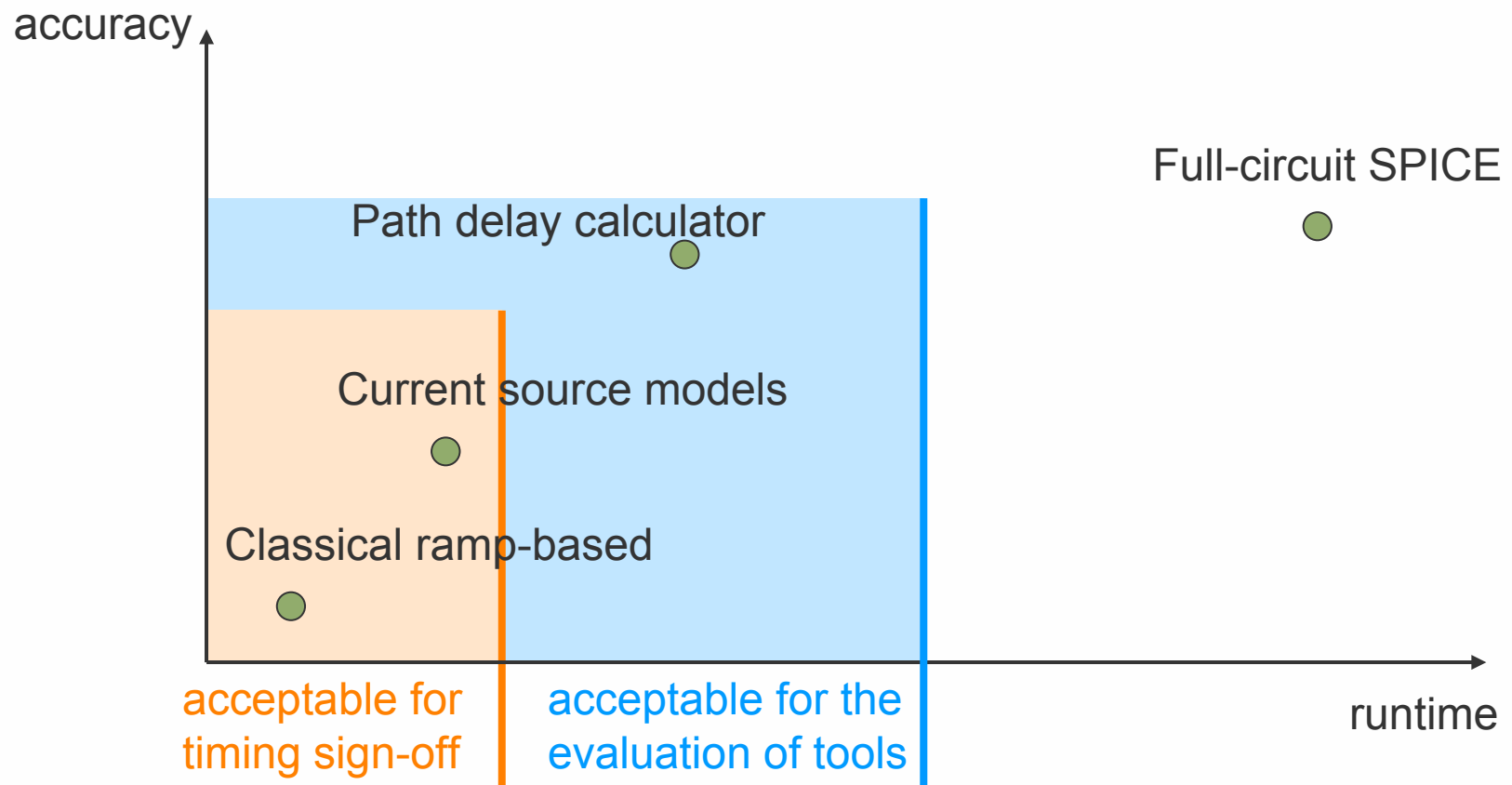

Considering Variations

Assumptions:


- Gaussian distributions
- Linear dependence on global and local process parameters

→ Canonical sum: $d = d_0 + \sum_i a_i \cdot \delta p_i$

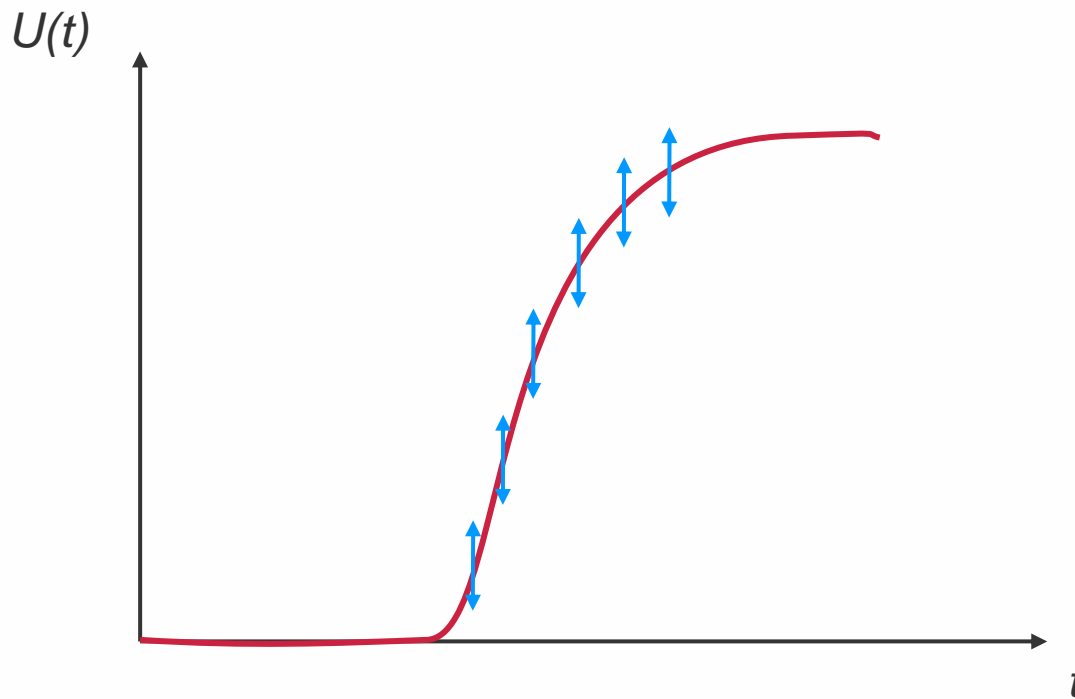Questions:

- How to model waveform variations ?
- How to obtain sensitivities a_i for these waveform variations?


Modeling Waveform Variations: Voltage Variations



$$V(t) = V_0(t) + \sum_i \chi_i(t) \cdot \delta p_i$$


Path-Based Propagation of Variations: Single Stage

Single Stage:

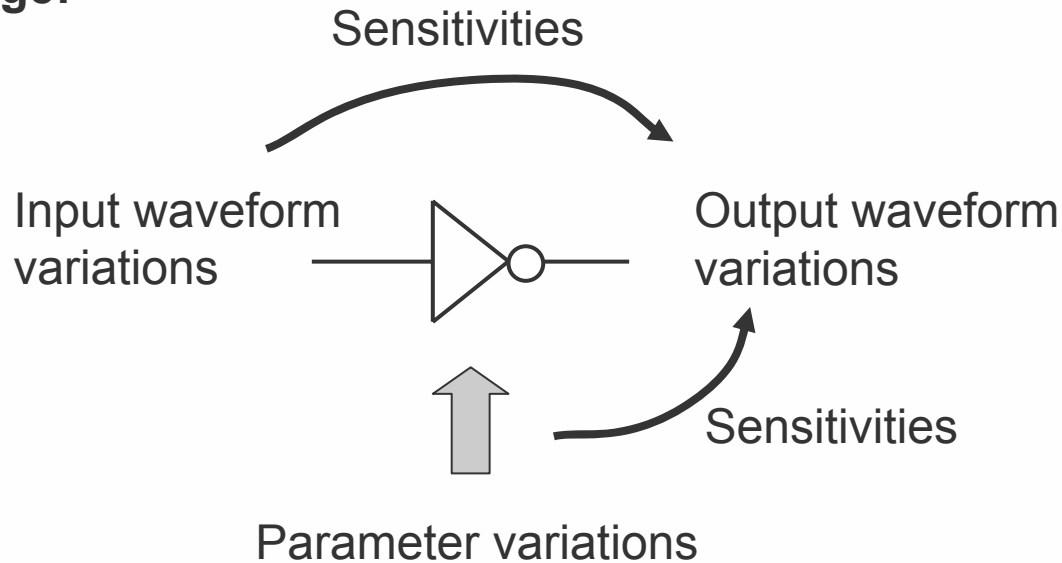


- Nominal simulation
- Sensitivities w.r.t. the input variations
- Sensitivities w.r.t. the gate parameter variations
- Addition of both influences

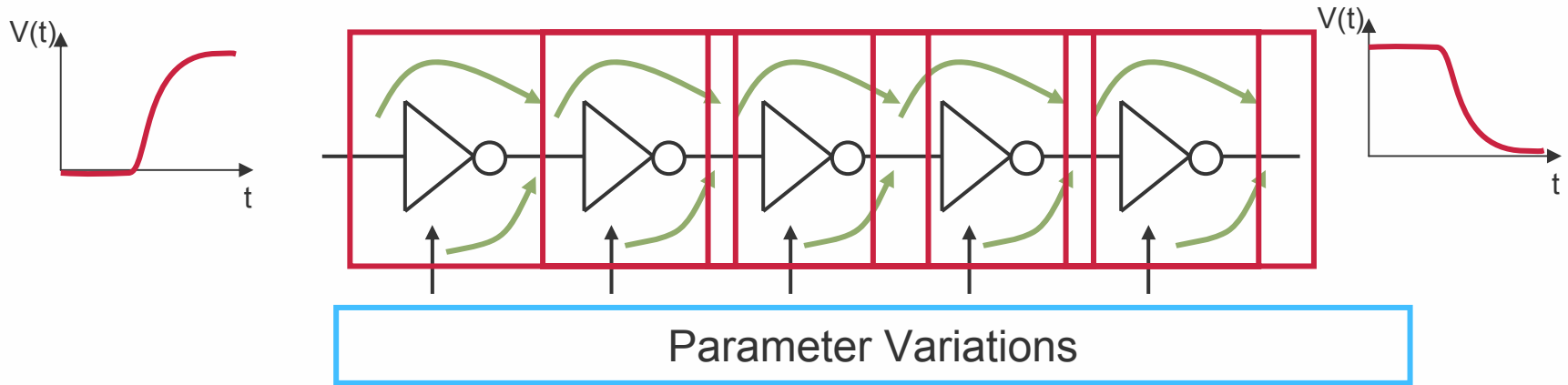Successive Path-based Propagation of Variations



Result:

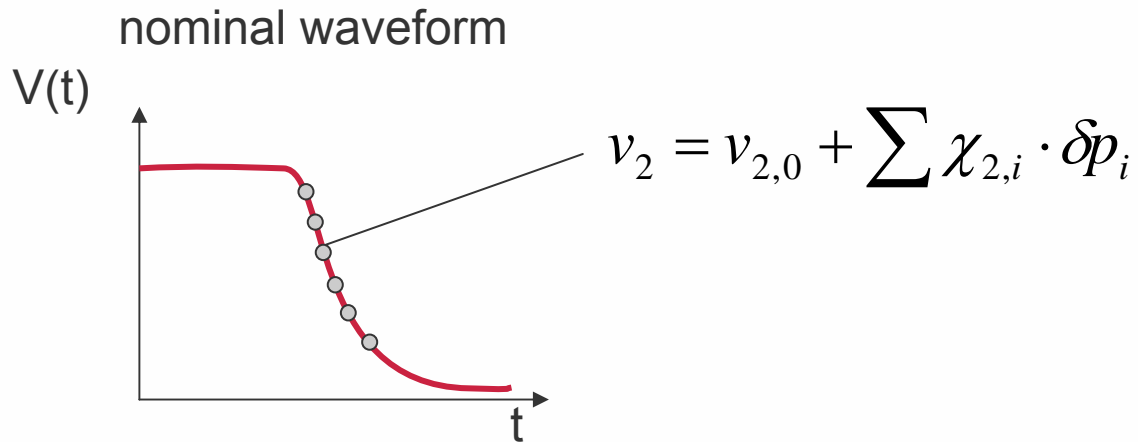

Results: Industrial Design


Paths with extracted post-layout parasitics including interconnects
(4 global, 2 local parameters)

#gates	#res/#cap	error σ_d	runtime	runtime 10,000 Monte Carlo	speedup
35	237/215	3%	15m23s	7d2h33m	665X
35	241/219	5%	15m27s	7d0h53m	655X
34	225/204	4%	15m7s	6d4h53m	590X
50	108/44	5%	23m20s	13d21h20m	857X

Outline


- Timing Analysis of Digital Circuits
- Statistical Waveform Variation Propagation
- Current Source Models (Transfer System Models)
- Summary

Evolution of Current Source Models

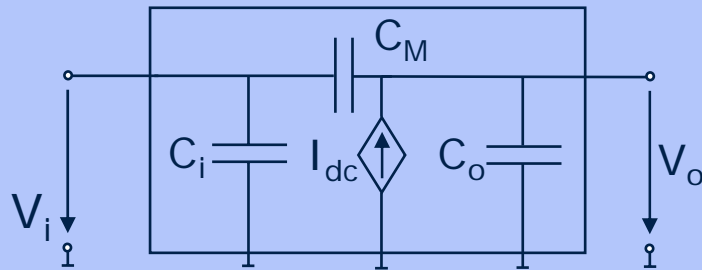


$$I_{dc} = f(V_i, V_o), C_i, C_o, C_M = \text{const.}$$

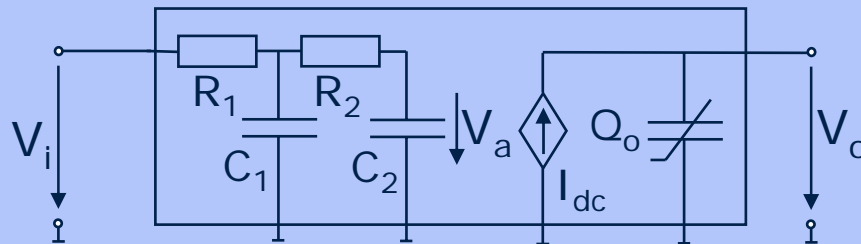DAC 2003, Croix, Wong:
Blade and razor: cell and interconnect delay analysis using current-based models



$$I_{dc} = f(V_a, V_o), Q_o = f(V_a, V_o)$$

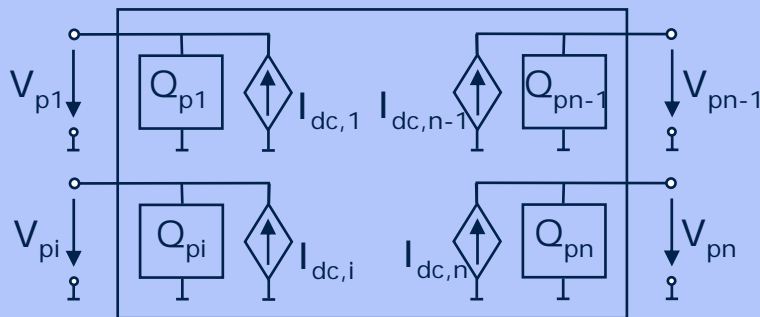2007 Transactions on VLSI, Li, Feng, Acar:
Characterizing Multistage Nonlinear Drivers and Variability for Accurate Timing and Noise Analysis



$$I_{dc,i} = f(V_{p1}, V_{p2}, \dots, V_{pn})$$

$$Q_{pi} = f(V_{p1}, V_{p2}, \dots, V_{pn})$$

DAC 2006, Amin et.al.:
A multi-port current source model for multiple-input switching effects in CMOS library cells


What do we really want ...?

$$i_2 = f(v_1, v_2)$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} j_1 \\ j_2 \end{bmatrix}$$

Transfer Conductance

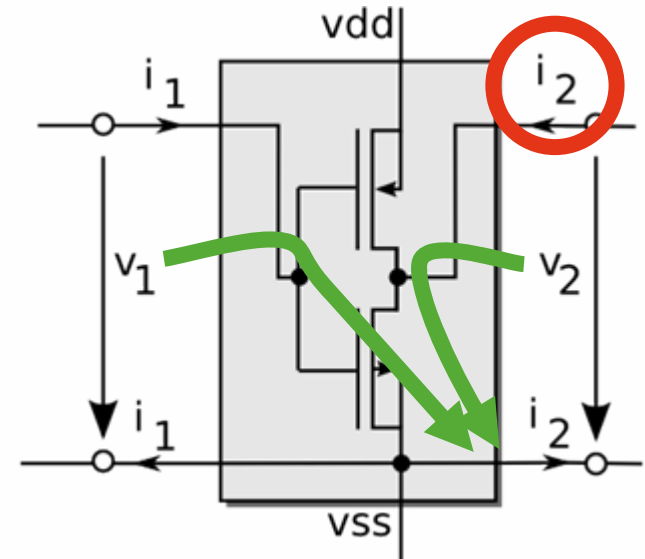- Replace nonlinear elements by equivalent circuits
- Calculate output current



Calculate transfer function on equivalent circuit

$$(\mathbf{G} + p\mathbf{C})\mathbf{x} = \mathbf{w}$$

$$\mathbf{T}\mathbf{x} = \mathbf{w}$$

$$x_i = \frac{\begin{vmatrix} \mathbf{T} & \mathbf{w} \\ -\mathbf{d}_i^t & 0 \end{vmatrix}}{\begin{vmatrix} \mathbf{T} & 0 \\ -\mathbf{d}_i^t & 1 \end{vmatrix}} = \frac{N(v_1, v_2, p)}{D(p)}$$


$$x_i = \frac{N(v_1, p)}{D(p)} + \frac{N(v_2, p)}{D(p)} + \frac{N_{DC}}{D(p)}$$

- Symbolically Solved
- Generally applicable
- Symbolic function independent of bias conditions
- Truncation




Account for nonlinearities by LUTs

$$i_2 = \frac{N(v_1, p)}{D(p)} + \frac{N(v_2, p)}{D(p)} + \frac{N_{DC}}{D(p)}$$

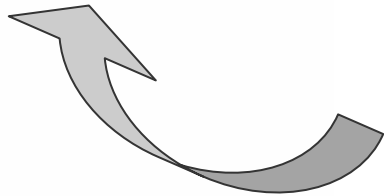
$$i_2 = \frac{\dots}{a \cdot p^2 + b \cdot p + c}$$




$$b(v_1, v_2) =$$

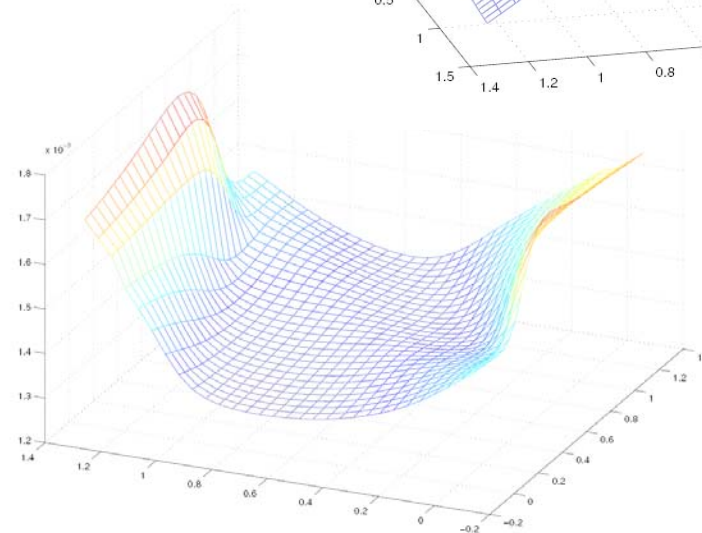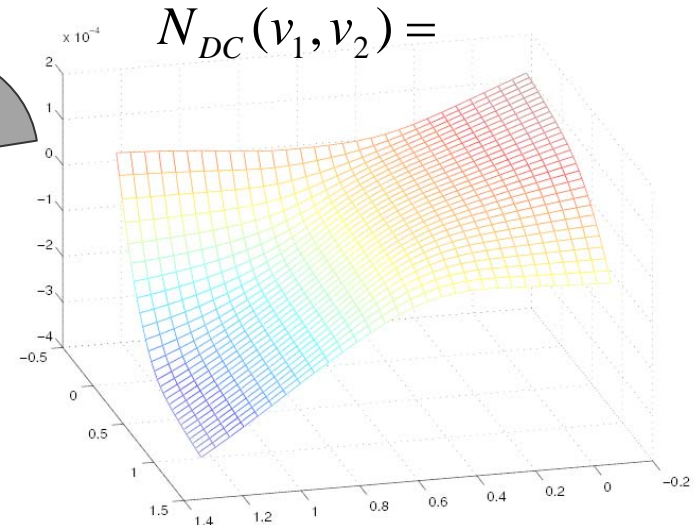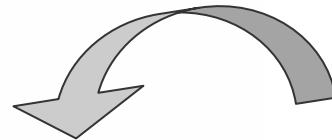

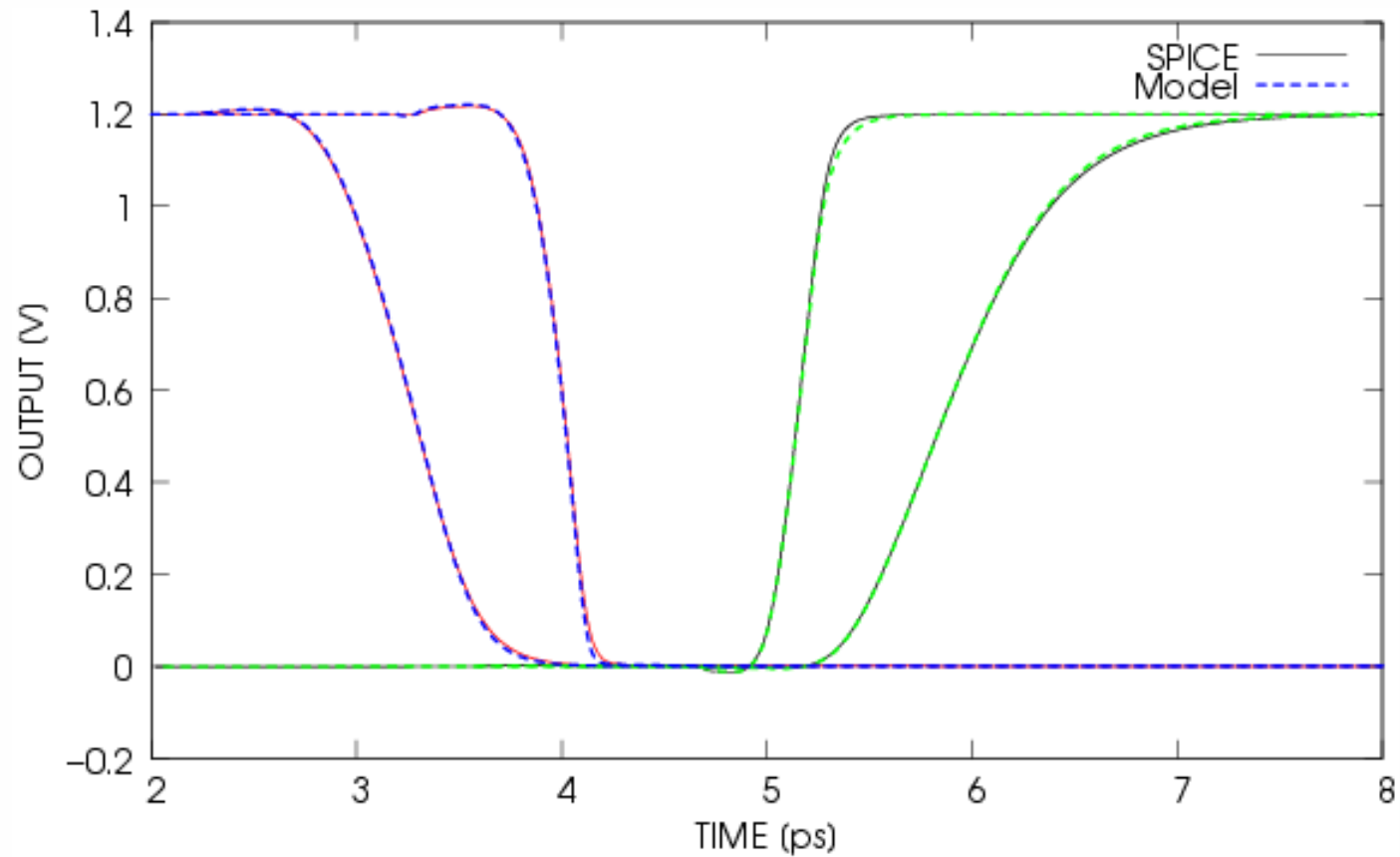Comparison to SPICE shows almost identical waveforms



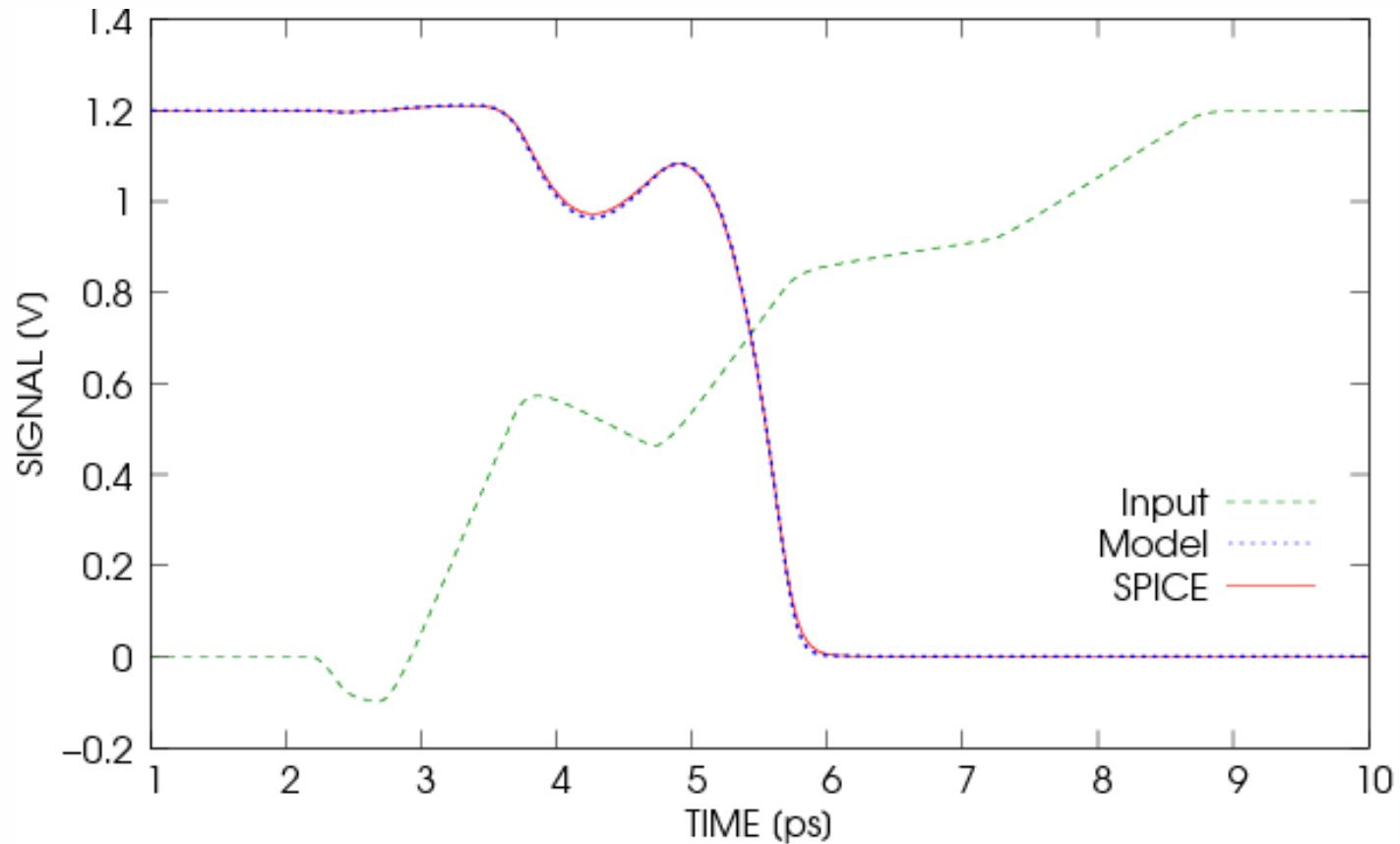Noisy input waveform also handled very accurately



Outline

- Timing Analysis of Digital Circuits
- Statistical Waveform Variation Propagation
- Current Source Models (Transfer System Models)
- Summary

Summary

- More detailed modeling for timing analysis required!
- Statistical modeling of waveform variations
- Structure-based Current Source Model
 - Symbolic (linear) transfer conductance function
 - Look-up Tables for coefficients
 - Simple to characterize (only DC measurements)

$$i_2 = \frac{N(v_1, p)}{D(p)} + \frac{N(v_2, p)}{D(p)} + \frac{N_{DC}}{D(p)}$$

